

Project 2: 16位ALU设计与实现

实验目的

1. 熟悉THINPAD硬件环境
2. 设计实现16位ALU及其控制器
3. 学习test bench写法以及仿真操作
4. 进一步锻炼硬件调试和测试能力

实验任务


1. 用VHDL设计实现16位ALU及其控制器
2. 使用THINPAD硬件平台测试

实验结果

仿真结果

对ALU进行行为级仿真


结果如图：

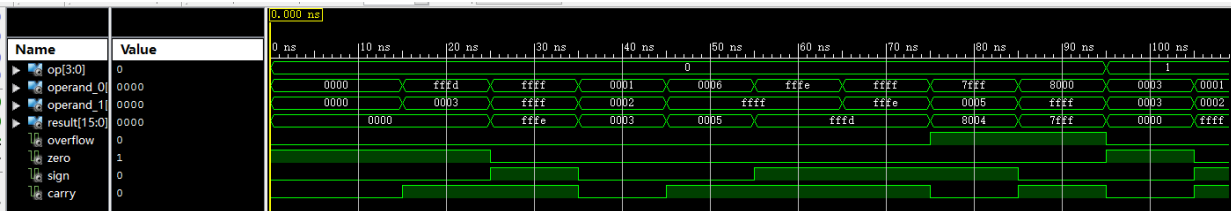

功能正确。

对整体设计进行行为级仿真

结果如图：

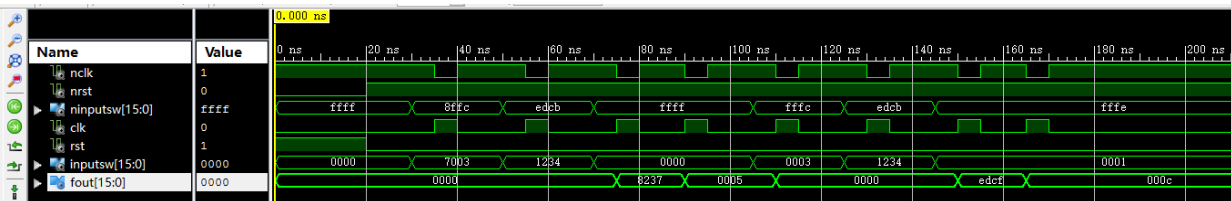

功能正确。

硬件测试结果

使用THINPAD硬件平台测试，功能正确。

源代码注解

ALU部分

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_unsigned.all;
use IEEE.numeric_std.all;
use work.constants.all;

entity alu is
    port
    (
        -- 操作码、操作数输入
        OP: in alu_op_t;
        OPERAND_0: in word_t;
        OPERAND_1: in word_t;

        -- 结果输出
        RESULT: out word_t;

        -- 标志位输出
        OVERFLOW: out std_logic;
        ZERO: out std_logic;
        SIGN: out std_logic;
        CARRY: out std_logic
    );
end;

architecture behavioral of alu is
    signal shamt: integer range 0 to word_msb;
    signal result_buff: word_t;

    signal adder_operand_0, adder_operand_1: word_t;
    signal adder_carry_in: std_logic;
    signal adder_buff: std_logic_vector(word_msb + 1 downto 0);
begin
    -- 移位数量的类型转换, 方便之后使用
    shamt <= to_integer(unsigned(OPERAND_1(3 downto 0)));

    -- 定义了一个加法器
    adder_buff <= ("0" & adder_operand_0) + ("0" & adder_operand_1) +
adder_carry_in;
    -- 计算输入给加法器的信号
    process(OP, OPERAND_0, OPERAND_1)
    begin
        adder_operand_0 <= OPERAND_0;
        -- 一个小选择器, 根据加减法选择不同的输入给加法器的操作数
        if OP = alu_add then
            adder_operand_1 <= OPERAND_1;
            adder_carry_in <= '0';
```

```

-- 对于减法的处理
else
    adder_operand_1 <= not OPERAND_1;
    adder_carry_in <= '1';
end if;
end process;

-- 计算进位（借位）、溢出标志
process(OP, OPERAND_0, OPERAND_1, adder_buff)
begin
    if OP = alu_add then
        -- 加法器的进位
        CARRY <= adder_buff(word_msb + 1);
        -- 如果 正+正=负, 或者 负+负=正, 则说明溢出了
        if (OPERAND_0(word_msb) = '0' and OPERAND_1(word_msb) = '0' and
adder_buff(word_msb) = '1')
            or (OPERAND_0(word_msb) = '1' and OPERAND_1(word_msb) = '1'
and adder_buff(word_msb) = '0') then
            OVERFLOW <= '1';
        else
            OVERFLOW <= '0';
        end if;
    elsif OP = alu_sub then
        -- 加法器的进位取反, 就是减法的借位信号
        CARRY <= not adder_buff(word_msb + 1);
        -- 如果 正-负=负, 或者 负-正=正, 则说明溢出了
        if (OPERAND_0(word_msb) = '0' and OPERAND_1(word_msb) = '1' and
adder_buff(word_msb) = '1')
            or (OPERAND_0(word_msb) = '1' and OPERAND_1(word_msb) = '0'
and adder_buff(word_msb) = '0') then
            OVERFLOW <= '1';
        else
            OVERFLOW <= '0';
        end if;
    else
        -- 其他操作进位和溢出都为0
        CARRY <= '0';
        OVERFLOW <= '0';
    end if;
end process;

-- 大选择器, 根据操作码选择对应的结果
process(OP, OPERAND_0, OPERAND_1, shamt, adder_buff)
begin
    case OP is
        when alu_add | alu_sub =>
            result_buff <= adder_buff(word_msb downto 0);
        when alu_and =>
            result_buff <= OPERAND_0 and OPERAND_1;
    end case;
end process;

```

```

        when alu_or =>
            result_buff <= OPERAND_0 or OPERAND_1;
        when alu_xor =>
            result_buff <= OPERAND_0 xor OPERAND_1;
        when alu_not =>
            result_buff <= not OPERAND_0;
        when alu_sll =>
            result_buff <= to_stdlogicvector(to_bitvector(OPERAND_0)
sll shamt);
        when alu_srl =>
            result_buff <= to_stdlogicvector(to_bitvector(OPERAND_0)
srl shamt);
        when alu_sra =>
            result_buff <= to_stdlogicvector(to_bitvector(OPERAND_0)
sra shamt);
        when alu_rol =>
            result_buff <= to_stdlogicvector(to_bitvector(OPERAND_0)
rol shamt);
        when others =>
            result_buff <= (others => 'X');
    end case;
end process;

-- 输出结果
RESULT <= result_buff;

-- 其余标志位计算
ZERO <= '1' when result_buff = zero_word else '0';
SIGN <= result_buff(word_msb);
end;

```

控制器部分

```

library IEEE;
use IEEE.std_logic_1164.all;
use work.constants.all;

entity controller is
    port
    (
        -- 单步时钟及复位键
        nCLK: in std_logic;
        nRST: in std_logic;
        -- 输入及输出
        nInputSW: in word_t;
        fout: out word_t
    );
end;

```

```

architecture behavioral of controller is
    component alu is
        port
        (
            -- 数据及操作码输入
            OP: in alu_op_t;
            OPERAND_0: in word_t;
            OPERAND_1: in word_t;

            -- 输出
            RESULT: out word_t;

            -- 标志位输出
            OVERFLOW: out std_logic;
            ZERO: out std_logic;
            SIGN: out std_logic;
            CARRY: out std_logic
        );
    end component;

    type state is (s_inputA, s_inputB, s_inputOP, s_outputFout,
s_outputFlag);
    signal current_state: state;

    signal clk, rst: std_logic;
    signal InputSW: word_t;

    signal OP: alu_op_t;
    signal OPERAND_0: word_t;
    signal OPERAND_1: word_t;
    signal result: word_t;
    signal output: word_t;
    signal OVERFLOW: std_logic;
    signal ZERO: std_logic;
    signal SIGN: std_logic;
    signal CARRY: std_logic;
begin
    clk <= not nCLK;
    rst <= not nRST;
    InputSW <= not nInputSW;

    fout <= output;

    -- 实例化ALU
    alu_inst: alu
    port map
    (
        -- 数据及操作码输入
        OP => OP,

```

```

    OPERAND_0 => OPERAND_0,
    OPERAND_1 => OPERAND_1,

    -- 输出
    RESULT => result,

    -- 标志位输出
    OVERFLOW => OVERFLOW,
    ZERO => ZERO,
    SIGN => SIGN,
    CARRY => CARRY
);

main : process(clk, rst)
begin
    -- 复位
    if rst = '1' then
        current_state <= s_inputA;
    elsif rising_edge(clk) then
        -- 状态转移的组合逻辑
        case current_state is
            -- 输入操作数A
            when s_inputA =>
                OPERAND_0 <= InputSW;
                current_state <= s_inputB;
            -- 输入操作数B
            when s_inputB =>
                OPERAND_1 <= InputSW;
                current_state <= s_inputOP;
            -- 输入操作码
            when s_inputOP =>
                OP <= InputSW(3 downto 0);
                current_state <= s_outputFout;
            -- 输出操作结果
            when s_outputFout =>
                current_state <= s_outputFlag;
            -- 输出标志位
            when s_outputFlag =>
                OPERAND_0 <= InputSW;
                current_state <= s_inputB;
            when others =>
                current_state <= s_inputA;
        end case;
    end if;
end process;

-- 根据当前状态，输出操作结果及标志位的组合逻辑
output_proc : process(current_state, result, OVERFLOW, ZERO, SIGN,
    CARRY)

```

```

begin
    case current_state is
        -- 输出操作结果
        when s_outputFout =>
            output <= result;
        -- 输出标志位
        when s_outputFlag =>
            output <= (others => '0');
            output(0) <= OVERFLOW;
            output(1) <= ZERO;
            output(2) <= SIGN;
            output(3) <= CARRY;
        when others =>
            output <= (others => '0');
    end case;
end process;
end;

```

面积优化

ALU中一个核心部件是加法器，虽然FPGA有硬件对加法器进行优化，但是一个16位加（减）法器仍然需要比较多的资源。如果把加法和减法的结果都计算出来之后再进行选择，就会综合出两个16位加（减）法器，考虑到我们目前并不需要同时知道加法和减法的结果，如果在计算之前对输入给加法器的操作数进行选择，那么加法和减法可以使用同一个加法器，这节约了硬件资源，同时减少了电路的面积。

虽然这个例子中我们在操作数之前额外加了一个选择器，但有的时候逻辑电路的面积减小了，布线延迟也会变小，速度反而会快。

思考题

ALU是组合逻辑电路还是时序逻辑电路？

是组合逻辑电路。

给定A和B初值，要求运算完毕结果写回B，再进行下一次运算，应增加什么电路？

需要添加寄存器（即一组触发器），以及修改状态机，增加写回的状态。